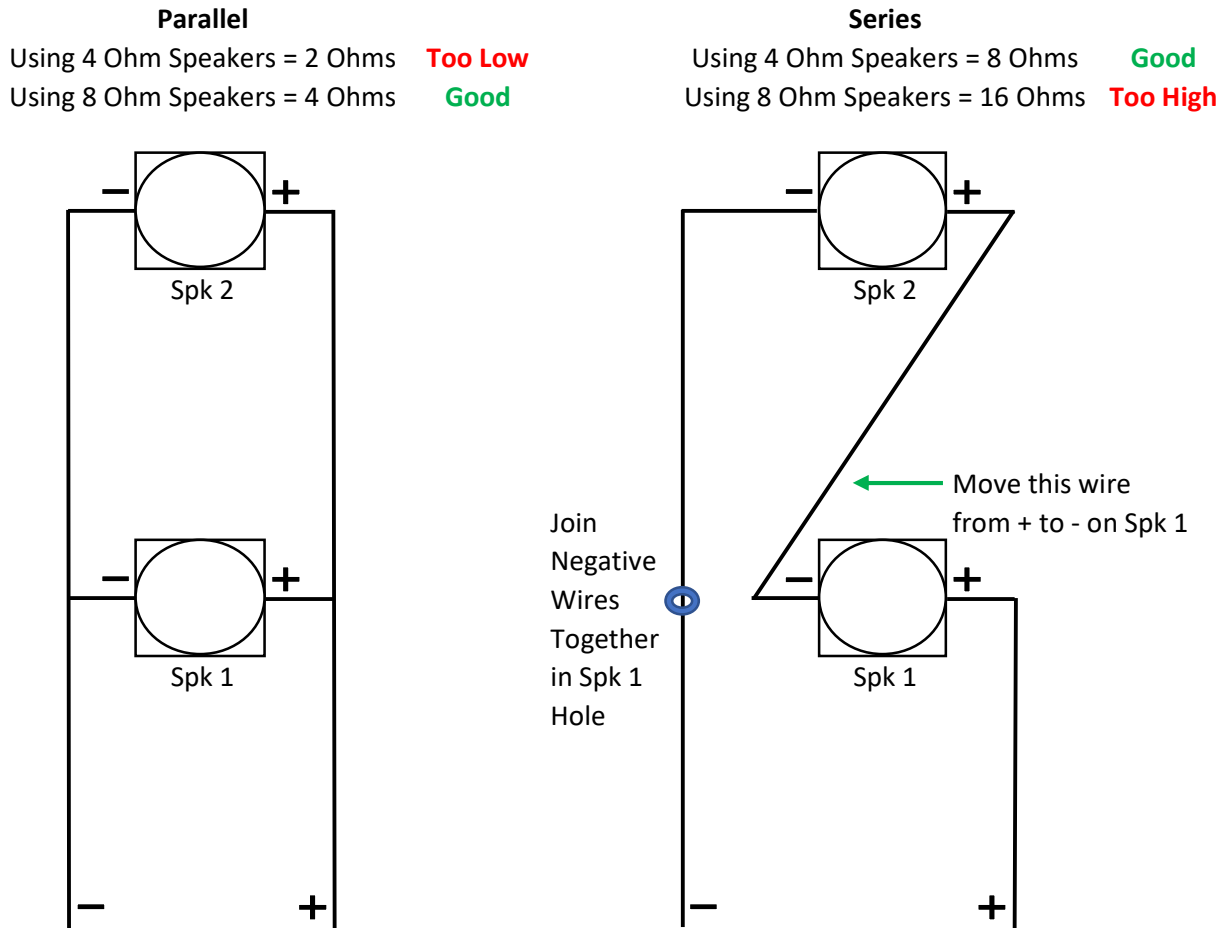


How to Rewire Speakers From Parallel to Series Using Existing Wiring



Notes:

Car Stereos and Amps are designed to run between 4 and 8 Ohms
If connected at 2 Ohms, they will get hot and eventually FAIL
If run over 8 Ohms will be very inefficient and have low volume
4 Ohms is the sweet spot for both efficiency and performance